



LAB 0: FPGA BASIC METHODOLOGY

James E. Stine, Jr.

Edward Joullian Endowed Chair in Engineering

Oklahoma State University

Electrical and Computer Engineering Department

Stillwater, OK 74078 USA

james.stine@okstate.edu

Objective

- The first lab has three main objectives:
 - The first objective is to learn how to design a basic digital design and verify it using a testbench.
 - The next objective is to implement it on your DSDB board and compare it to what you get from simulation.
 - The last objective is to understand the lab structure and report.
- History has indicated many people will wait – you cannot complete any lab overnight, be forewarned.
 - We will revisit lab report later today.
 - Also, you probably cannot finish this lab in one lab session.


Things to keep in mind

- Start early and work with your partner to get things done quickly.
 - **Communication** is key to a good relationship.
 - Do not ask what I can do, just jump in and contribute even if you duplicate work.
- Labs are due one week after the lab is complete.
 - For lab 0, this Friday February 4
- Try to schedule the last week of lab for writing up your work, so you basically only have 2 weeks to complete this lab.
 - Back up often and work upwards (inverted pyramid).
 - Ask questions on slack or in person **early!**
 - Know we are here to help – post screenshots/questions on slack or stop by.

Basics

- For this laboratory, we will be using the ELVIS III board.
- We have made most of it very simple if you follow the procedure and understand what is going on.
- I have uploaded a version of the files that include a directory with the items you need to copy over to your working area once your simulation works.
- There is also simulation that I will demonstrate how to make sure this is working **before** you go to the ELVIS board.
- Make sure you have a DSDB board at your desk before you begin.
 - Ask your TA to install it, if its not there.

DSDB

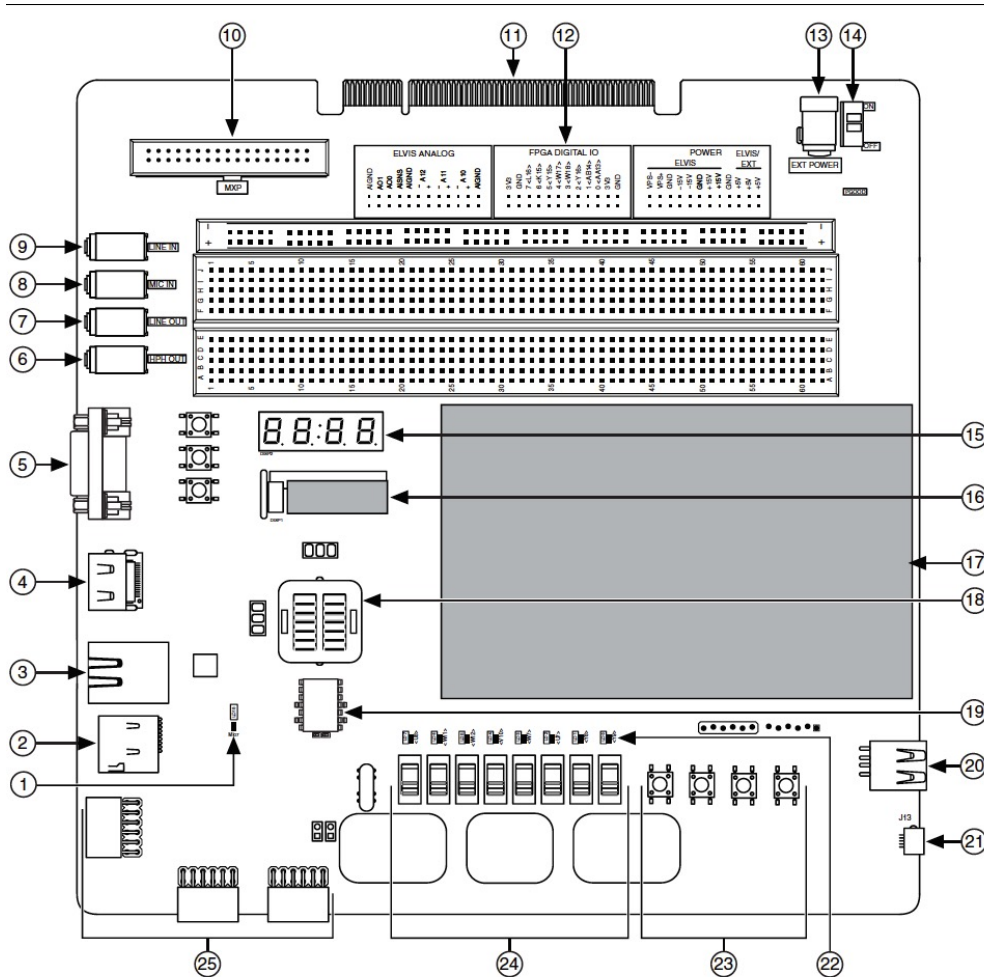


18: Zynq XC7Z020-1CLG484C
with included Heat Sink


All of the FPGA pins are
accessible via the DSDB board
either through the schematic or
attaching to the debugger

Field-Programmable Gate Arrays

 - Logic blocks
 - To implement combinational and sequential logic
- Interconnect
 - Wires to connect inputs and outputs to logic blocks
- I/O blocks
 - Special logic blocks at periphery of device for external connections
- Key questions:
 - How to make logic blocks programmable?
 - How to connect the wires?
 - *After the chip has been fabbed or fabricated!*



Evolution of FPGA architectures

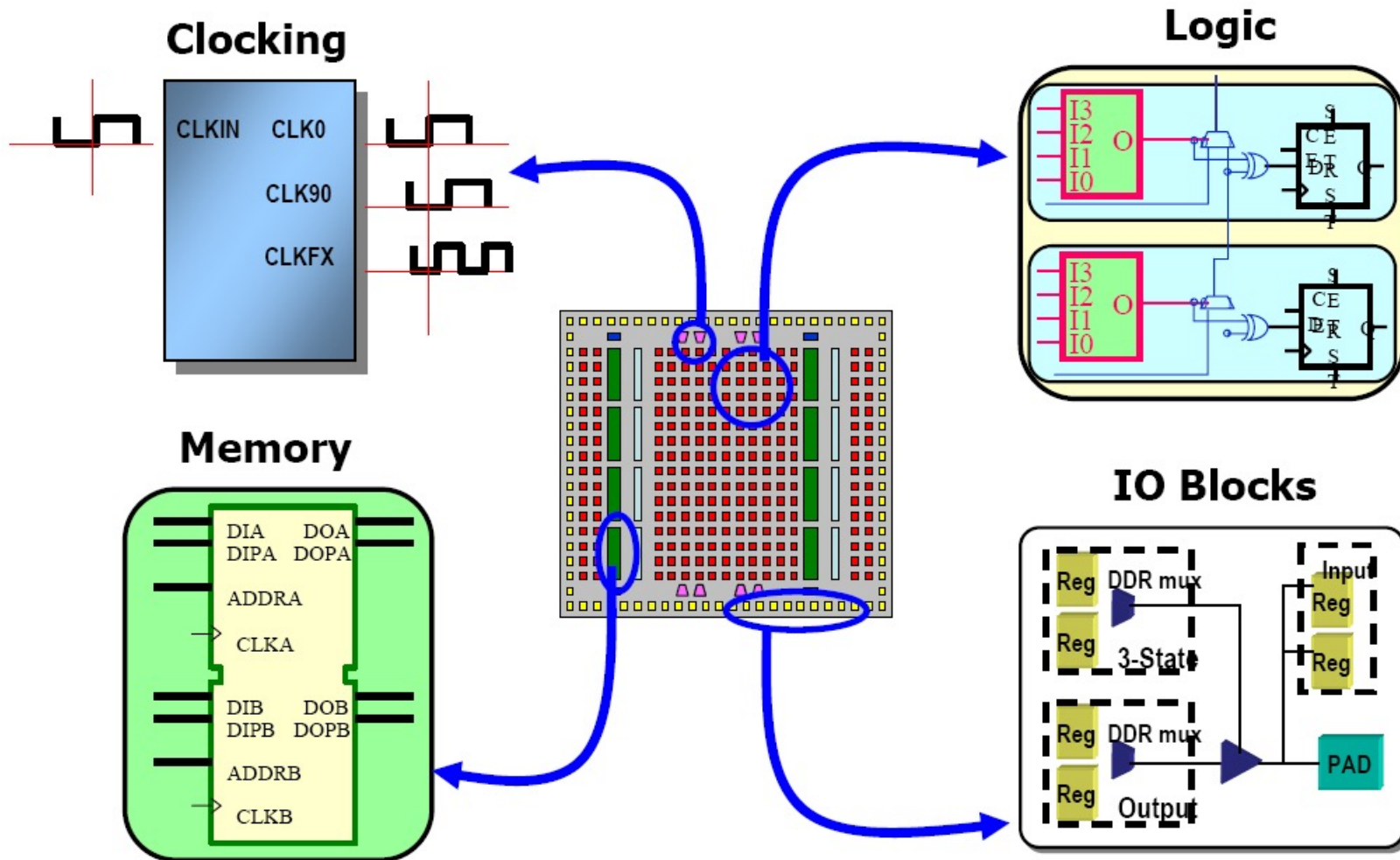

Tasks

- Download labs0.zip from Canvas
 - Unzip your files somewhere (e.g., Desktop)
- First test sillyfunction SystemVerilog with ModelSim
 - Navigate to your unzipped files.
 - Try compiling silly.sv with: `vlog silly.sv`
 - Examine testbench with text editor to see what is happening
 - Simulate and Examine with ModelSim: `vsim -do silly.do`
- Implement the full adder (3 bits in, 2 bits out) in SystemVerilog
 - Boolean Logic is given and implement new SystemVerilog file using silly.sv as a template
 - Modify the silly_tb.sv for the FA (Do not try to reinvent the wheel – just change the silly items and the vectors)
 - Test all 8 inputs!
 - Simulate with ModelSim and Check that it works
 - You might want to write down the correct truth table on paper
 - Examine that the truth table matches the waveform for every combination ($2^3 = 8$ combinations)
- Much of these tasks can be done on your own outside or inside laboratory

HDL to Gates

- **Simulation**

- Inputs applied to circuit
- Outputs checked for correctness
- Millions of dollars saved by debugging in simulation instead of hardware



- **Synthesis**

- Transforms HDL code into a *netlist* describing the hardware (i.e., a list of gates and the wires connecting them)


- **Verification**

- Verifying the forward translation of synthesis is indeed what you started with

Demo of Simulation


- Let's try to simulate `silly.do`

MGC ModelSim vsim window

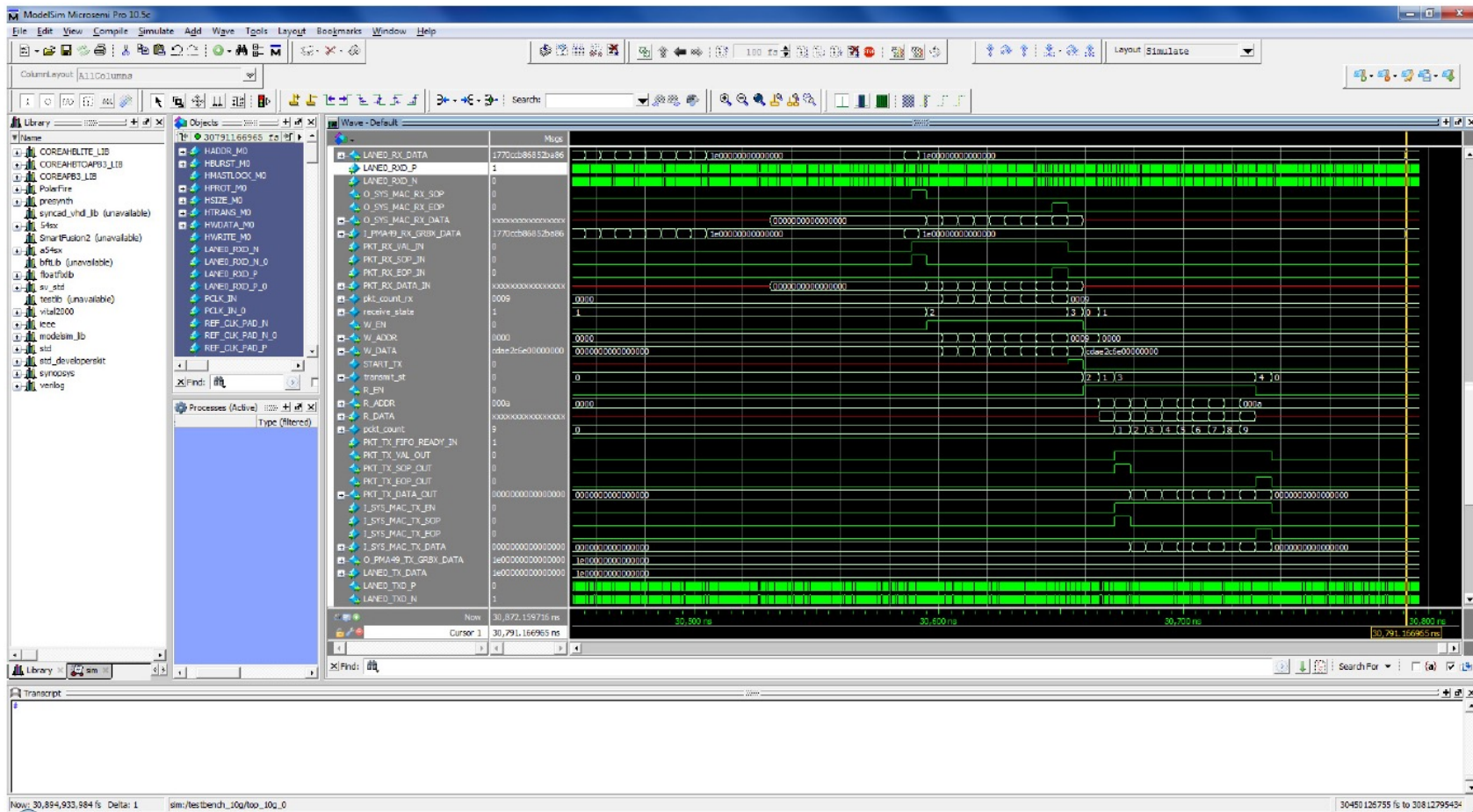

Full Adder

Half Adder

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

Full Adder

 

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

- The full adder is sometimes called the basic building block of any computation.
- Specifically, the full adder is sometimes called a (3,2) counter because it counts the numbers of inputs that are 1.
- Use the basic silly module discussed in Lecture 3 for building the full adder.
- Make sure you test it thoroughly for all 8 combinations in your simulation with a testbench before you go to your DSDB board.

Instantiating designs

```
module and3(input  logic a, b, c,  
            output logic y);  
    assign y = a & b & c;  
endmodule
```

```
module inv(input  logic a,  
            output logic y);  
    assign y = ~a;  
endmodule
```

```
module nand3(input  logic a, b, c  
             output logic y);  
    logic n1;                                // internal signal  
    and3 andgate(a, b, c, n1);              // instance of and3  
    inv  inverter(n1, y);                   // instance of inv  
endmodule
```

- When creating HDL, you instantiate other designs in your higher-level HDL.
- This allows you to build bigger and better designs.
- It uses hierarchy to make more complex designs.
- andgate is our instantiated name

Debugging?

- You will be implementing your design on your FPGA on the National Instruments DSDB board.
 - The implementation will be inside the silicon which you cannot see.
 - So, how do you figure out if something is working? How do you tell something does not work the way you expected it to?
- Use debugging techniques!
 - This includes switches, LEDs, push buttons to help you examine what is happening with the board.
 - Try to use as many LEDs as you can to see what is on and what is off.
 - Use your brain to figure out possible problems.

Implementation on DSDB

- Once you simulate your design, you should hook up to the DSDB.
- Inside your `lab0.zip` there should be a Demo program.
 - Unzip and open with Vivado
- Modify the `top_demo.sv` to instantiate your “working” SV and hook up inputs and outputs to things you can see on the DSDB:
 - Hook your input/output of your instantiated design to debugging items (e.g., LEDs).
 - Test all 8 possible combinations of your full adder to make sure its working as expected.

Port	Type	Description
<code>sw[3:0]</code>	Input	push buttons (#23)
<code>btn[7:0]</code>	Input	SPDT slide switches (#24)
<code>led[7:0]</code>	Output	Light Emitting Diodes (LEDs) (#22)

Table 1: Ports Used for Lab 0

- Using Vivado (which is Xilinx’s synthesis and place/route tool) - this should be on your desktop in ENDV 360 to run
 1. Run Synthesis
 2. Run Implementation
 3. Generate Bitstream
- Per the `lab0.pdf`, download to the board using the Hardware Manager


Check on DSDB board

- **DO NOT TRY AN IMPLEMENTATION ON YOUR DSDB BOARD UNTIL IT WORKS IN SIMULATION!**
 - It takes several minutes to go through the three steps inside Vivado (e.g., synthesis).
 - You want to hopefully do the implementation once or twice.
 - Use your debugging items and your brain to make sure things are working.
- Check on DSDB board whether things work (check against the truth table).
 - Use the Light-Emitting Diodes (LEDs) to make sure all 8 possible cases match your simulation from ModelSim and theory.
- If you like, save any output from the Vivado screen for your report
 - e.g., Schematic, Implementation Results
- Write your report!

Lab Report

- The lab report should be simple and efficient with 5 sections (much of this information is in the rubric)

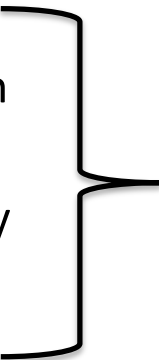- Section 1: Introduction
- Section 2: Baseline Design
- Section 3: Design
- Section 4: Testing Strategy
- Section 5: Evaluation
- Team Evaluation



One report for each team but both team members **must** submit a Team Evaluation to get full credit!

- Check Lab Report Formats
 - Use a 10-pt font
 - Your report should be a **maximum** of four pages not including figures.
 - Figures and Tables go in the Appendix
- Do not read too much into the rubric: just get it done to showcase what you did.

Last-minute Items

- Challenge yourself and get things done early!
 - Last semesters students waited until the second week when its too late!
 - You may have to visit the lab more than once! (i.e., you cannot always complete your work in one lab session)
- Submit all HDL, scripts, lab reports, and team evaluation for each member through Canvas.
 - Do not forget your HDL, testbenches, DO files or you will get a deduction.
 - Also, do not forget the team evaluation from each team member!!!!
- Believe in yourself – we all tend to be negative about our abilities (don't!)
 - You can do it!
 - OSU students are the best!
- Enjoy the opportunity!

